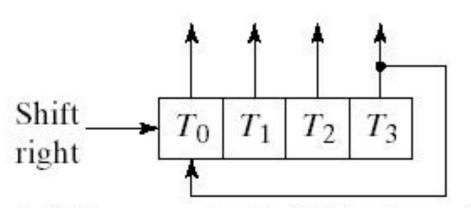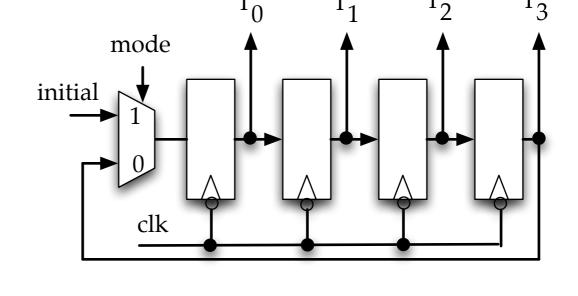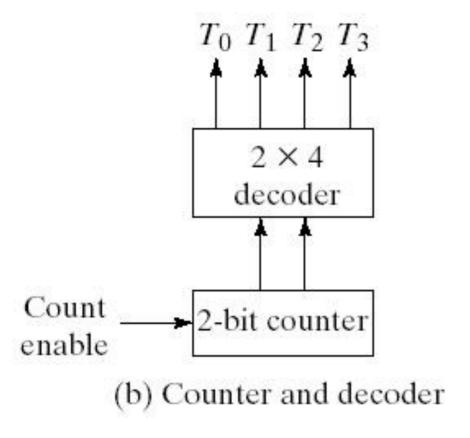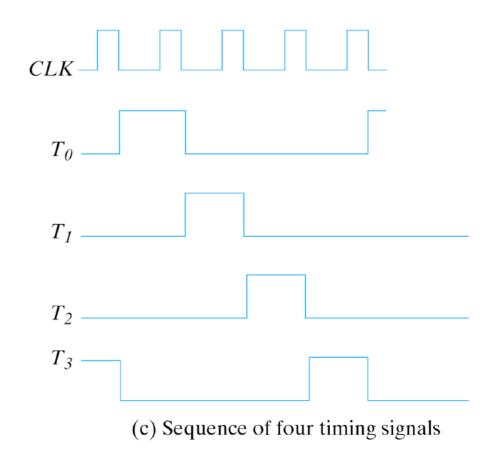# Ring Counter Applications

(a) Ring-counter (initial value = 1000)

(b) Counter and decoder

(c) Sequence of four timing signals